

N26F300
VLSI SYSTEM DESIGN
(GRADUATE LEVEL)

Processors and Peripherals

Outline


2

- **Processor**
- **Custom processor – GCD example**
- **Peripherals**

[Material partly adapted from Embedded System Design by F. Vahid & T. Givargis]


Design metric competition -- improving one may worsen others

3

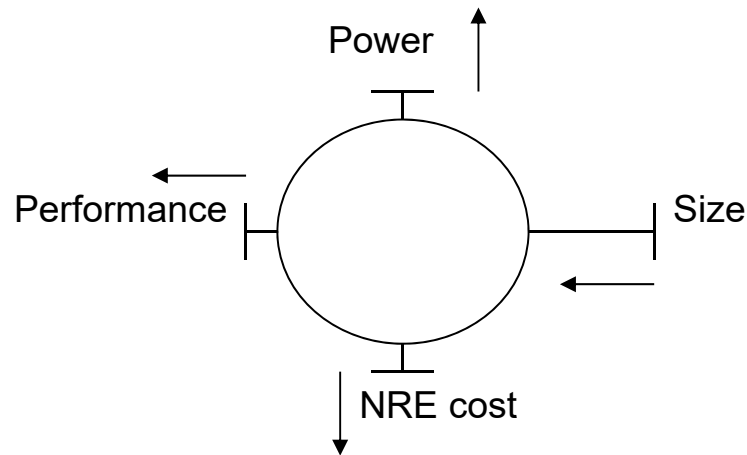

Expertise with both **software** and **hardware** is needed to optimize design metrics

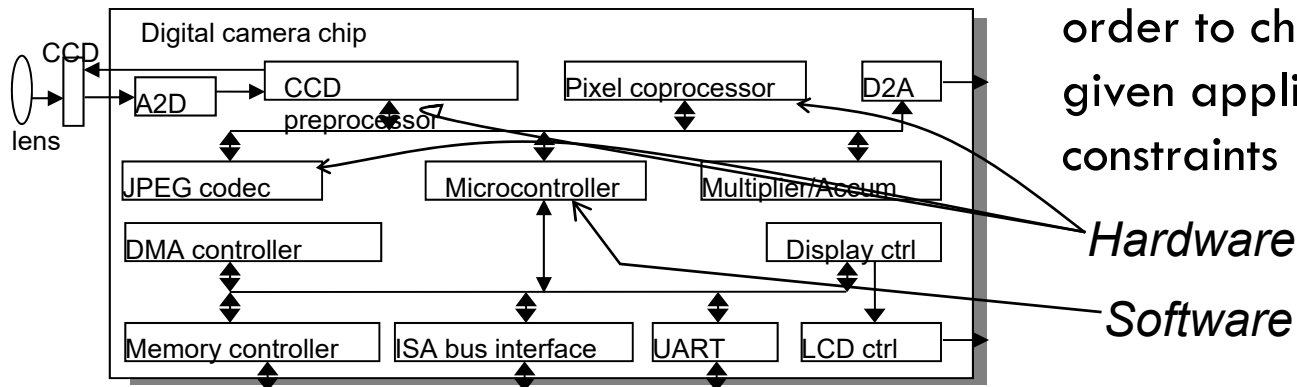
- Not just a hardware or software expert, as is common
- A designer must be comfortable with various technologies in order to choose the best for a given application and constraints



Processor technology

4

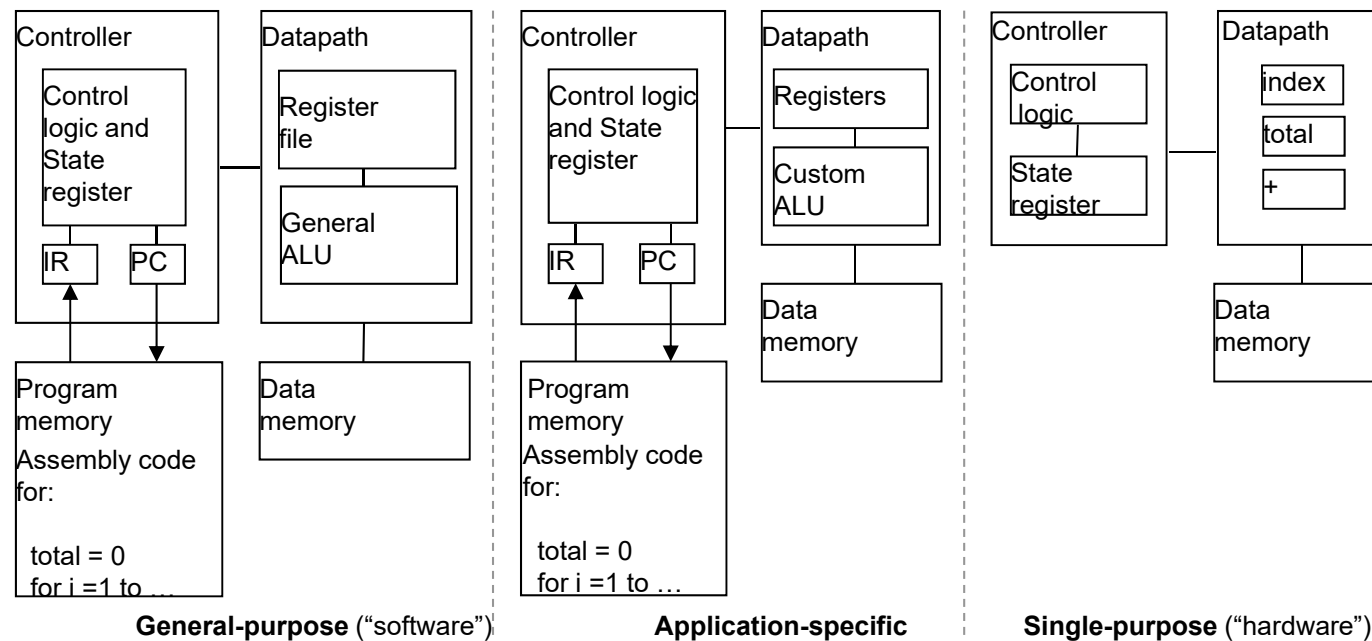- The architecture of the computation engine used to implement a system's desired functionality
- Processor does not have to be programmable
 - ▣ “Processor” *not* equal to general-purpose processor



Processor technology


5

- Processors vary in their customization for the problem at hand




Desired
functionality

 
```
total = 0
for i = 1 to N loop
  total += M[i]
end loop
```



General-
purpose
processor

 

Application-specific
processor

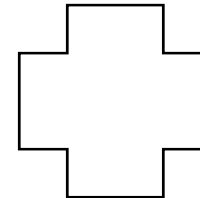


Single-
purpose
processor

General-purpose processors

6

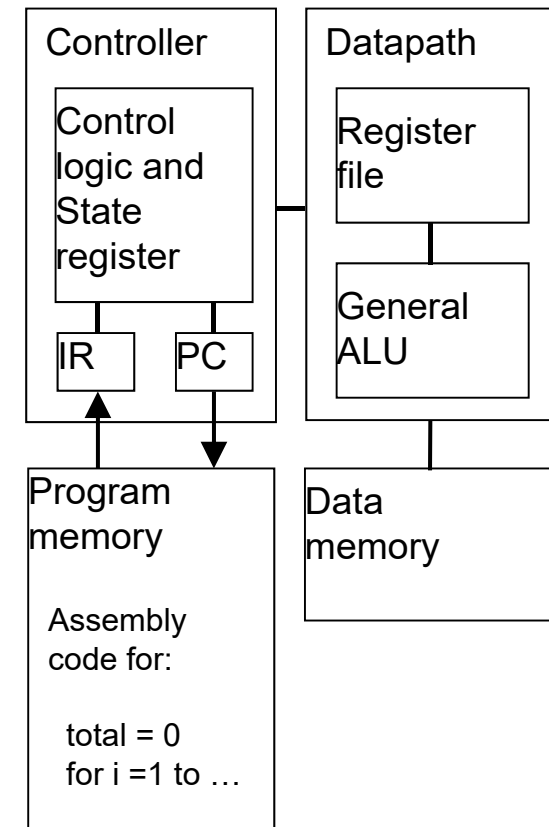
- Programmable device used in a variety of applications
 - ▣ Also known as “microprocessor”
- Features
 - ▣ Program memory
 - ▣ General datapath with large register file and general ALU
- User benefits
 - ▣ Low time-to-market and NRE costs
 - ▣ High flexibility
- “Pentium” the most well-known, but there are hundreds of others



Single-purpose processors

7

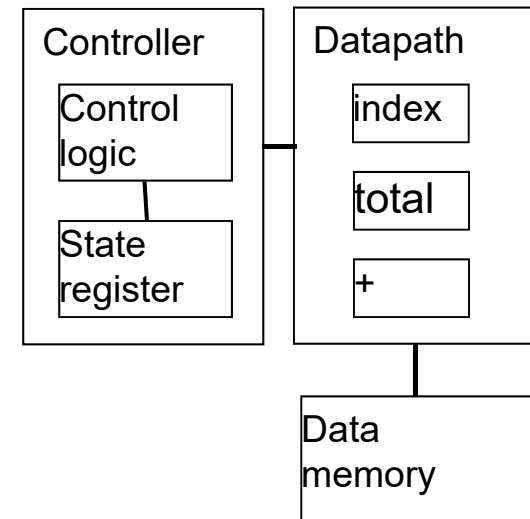
- Digital circuit designed to execute exactly one program
 - ▣ a.k.a. coprocessor, accelerator or peripheral
- Features
 - ▣ Contains only the components needed to execute a single program
 - ▣ No program memory
- Benefits
 - ▣ Fast
 - ▣ Low power
 - ▣ Small size



Application-specific processors

8

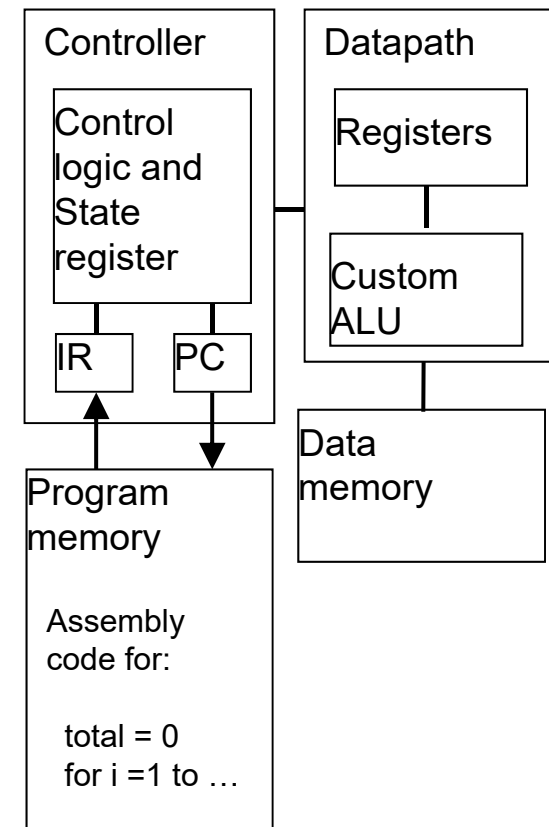- Programmable processor optimized for a particular class of applications having common characteristics
 - ▣ Compromise between general-purpose and single-purpose processors
- Features
 - ▣ Program memory
 - ▣ Optimized datapath
 - ▣ Special functional units
- Benefits
 - ▣ Some flexibility, good performance, size and power




Independence of processor and IC technologies

9

□ Basic tradeoff

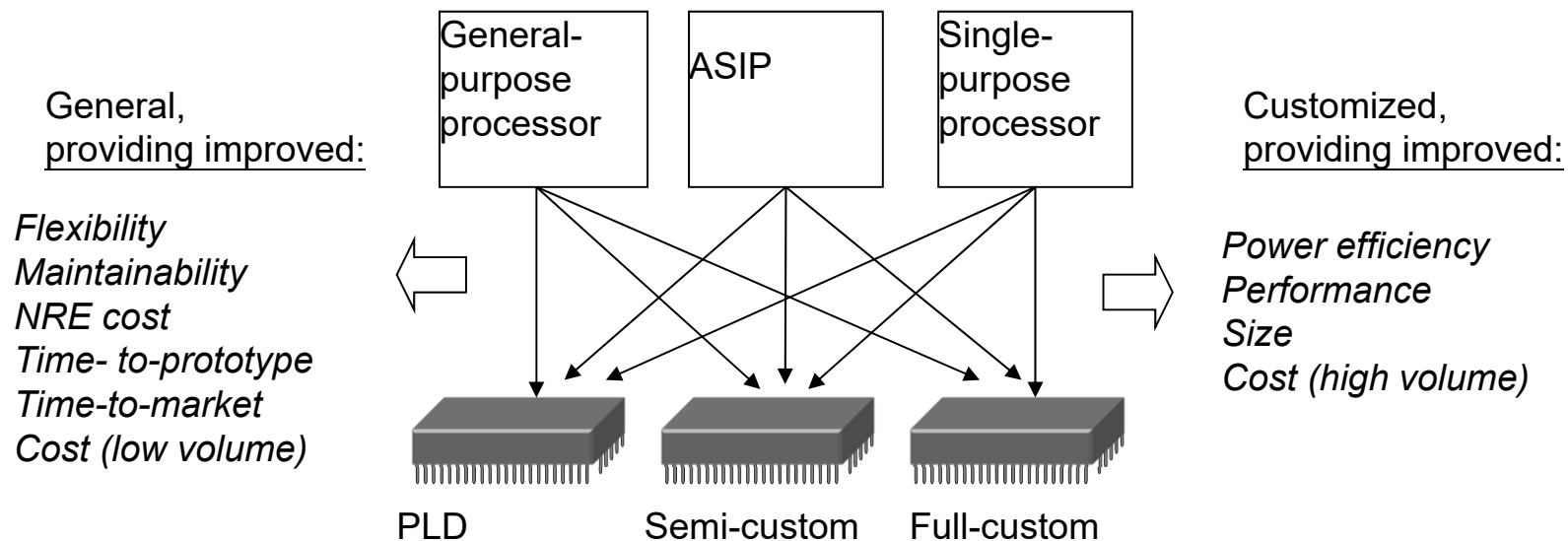- General vs. custom
- With respect to processor technology or IC technology
- The two technologies are independent



Custom Processor


10

□ Processor

- Digital circuit that performs a computation tasks
- Controller and datapath
- General-purpose: variety of computation tasks
- Single-purpose: one particular computation task
- Custom single-purpose: non-standard task

□ A custom single-purpose processor may be

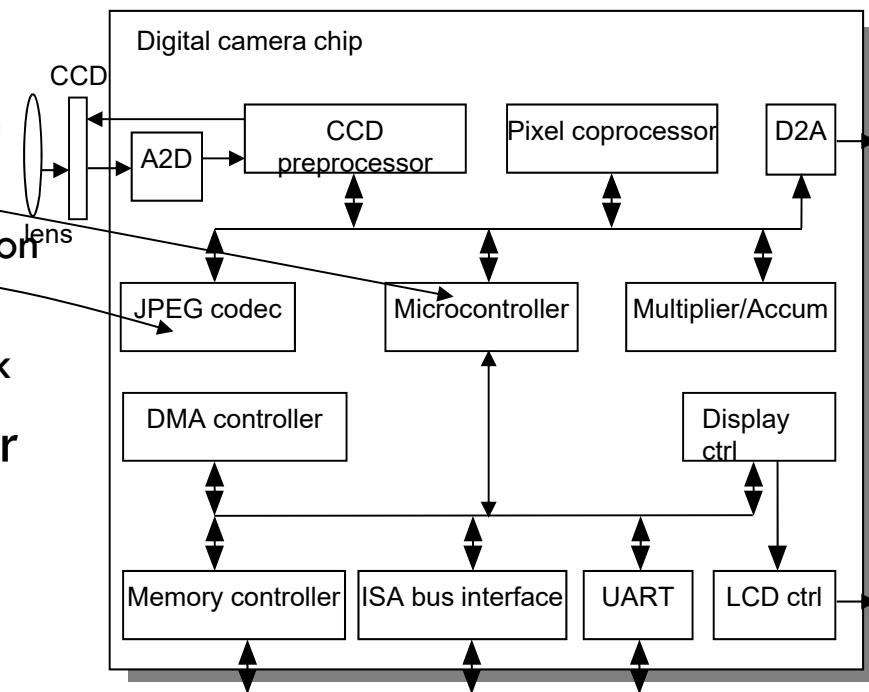- Fast, small, low power
- But, high NRE, longer time-to-market, less flexible




Example: greatest common divisor

11

- First create algorithm
- Convert algorithm to “complex” state machine
 - ▣ Known as FSMD: finite-state machine with datapath
 - ▣ Can use templates to perform such conversion

(a) black-box view

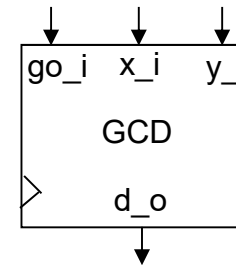


(b) desired functionality

```

0: int x, y;
1: while (1) {
2:   while (!go_i);
3:   x = x_i;
4:   y = y_i;
5:   while (x != y) {
6:     if (x < y)
7:       y = y - x;
8:     else
7:       x = x - y;
9:   }
9:   d_o = x;
}
    
```

(c) state diagram

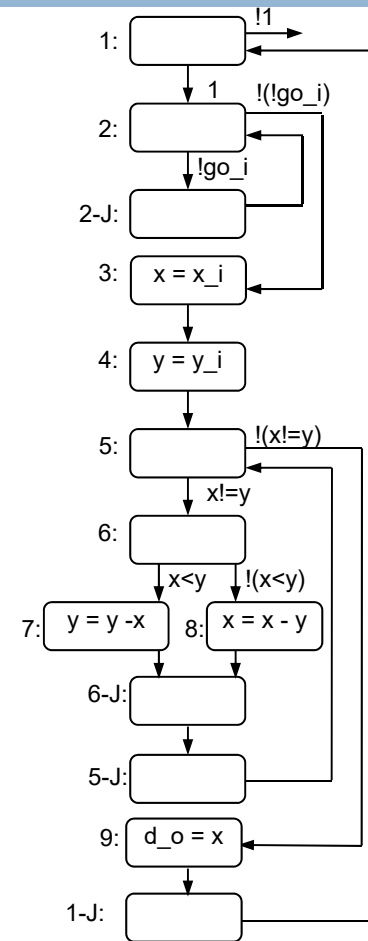


State diagram templates

12


Assignment statement

a = b
next
statement

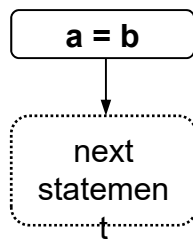


Loop statement

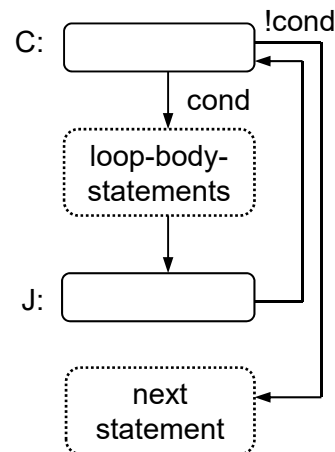while (cond) {
loop-body-
statements
}
next statement



Branch statement


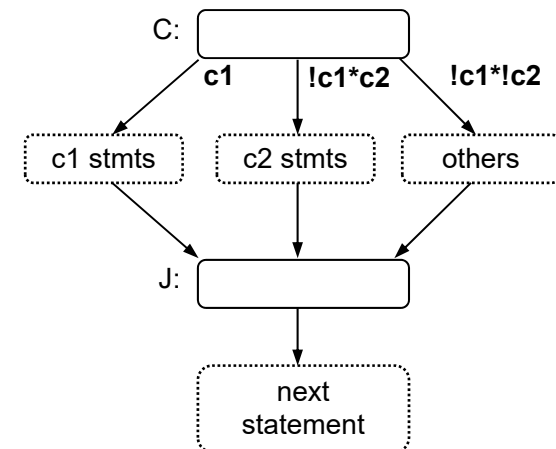
if (c1)
c1 stmts
else if c2
c2 stmts
else
other stmts
next statement



Creating the datapath



13

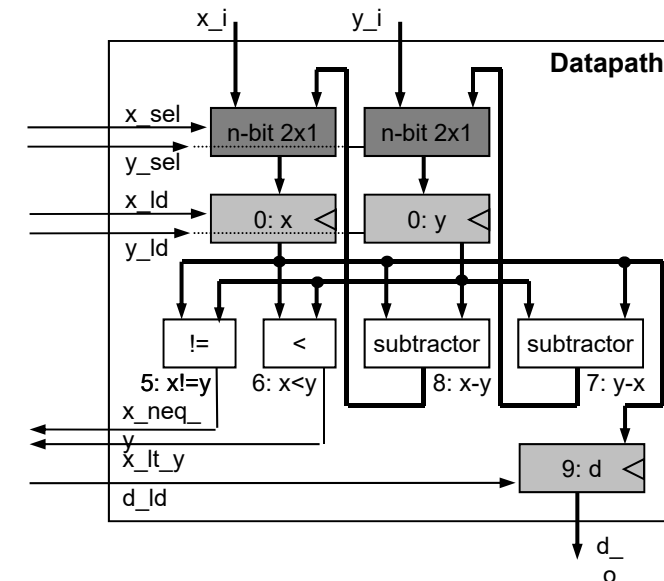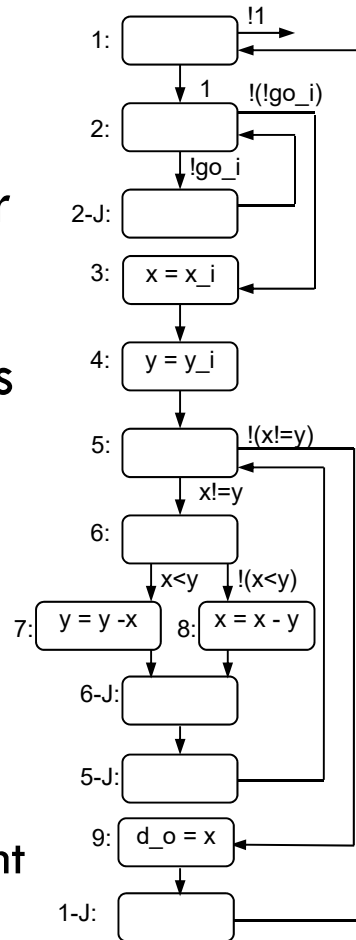- Create a register for any declared variable
 - Based on reads and writes
 - Use multiplexors for multiple sources
- Create unique identifier
 - for each datapath component control input and output




Creating the controller's FSM

14


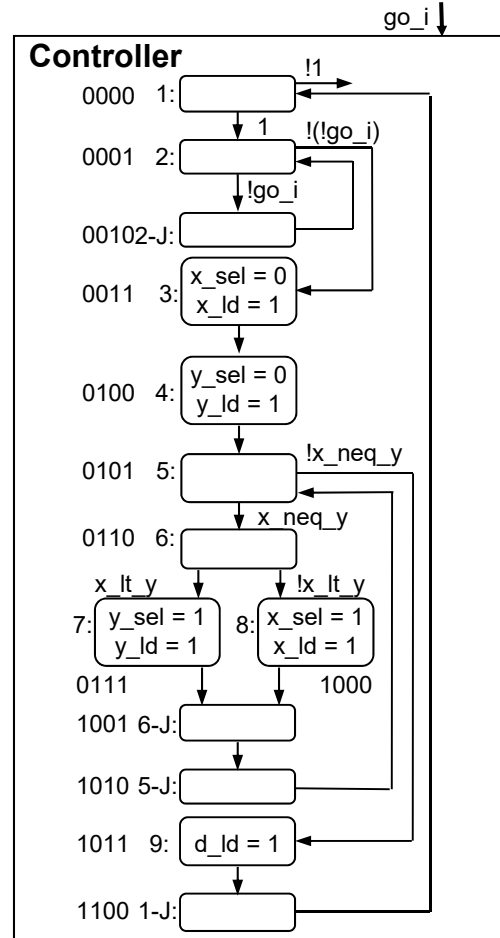
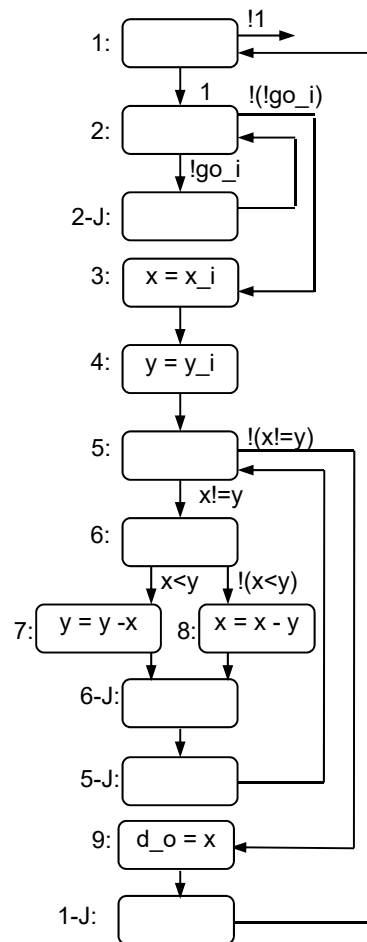


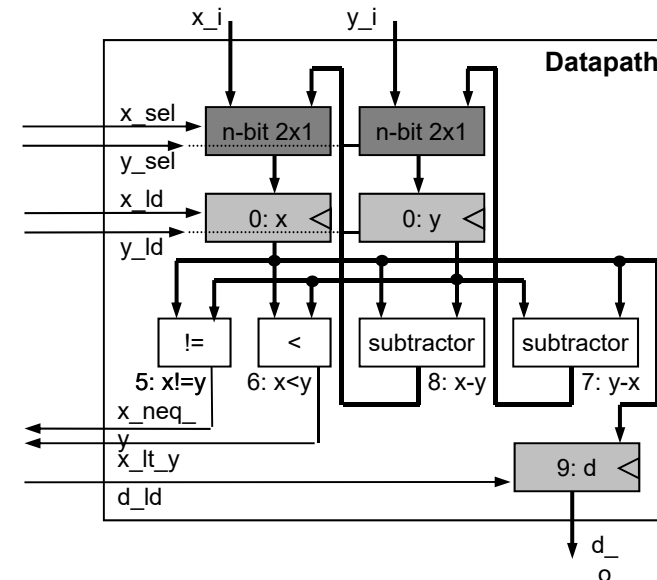- Same structure as FSMD
- Replace complex actions/conditions with datapath configurations



Splitting into a controller and datapath

15

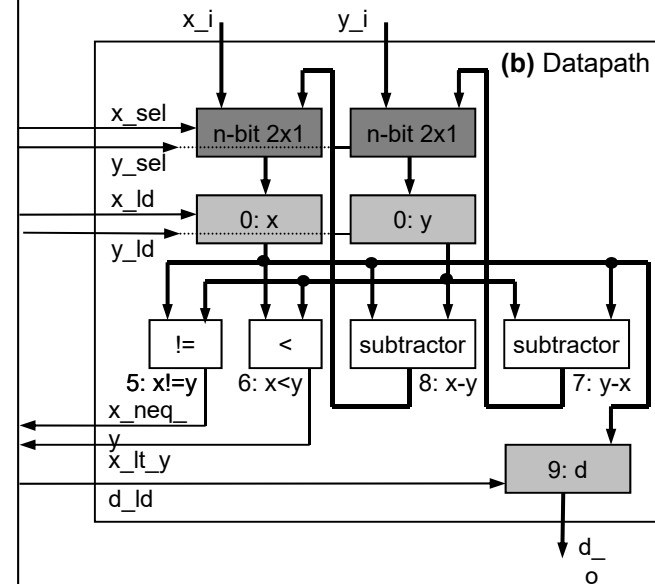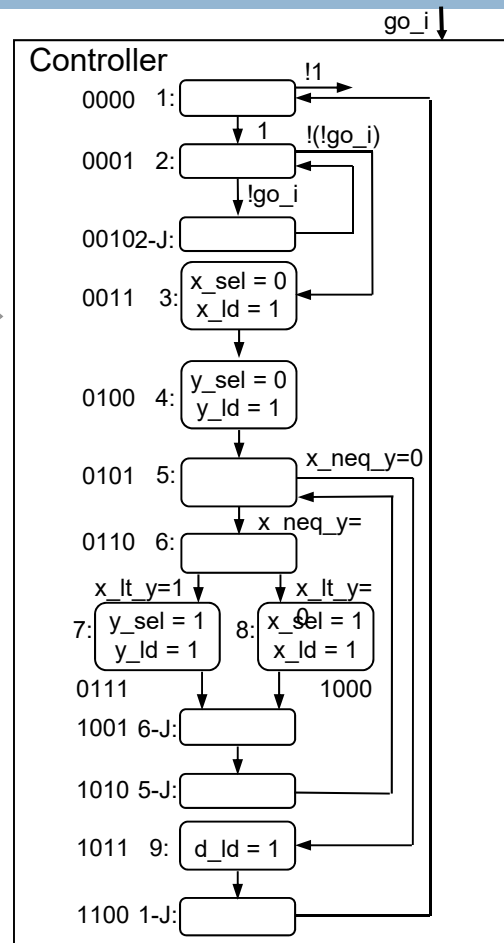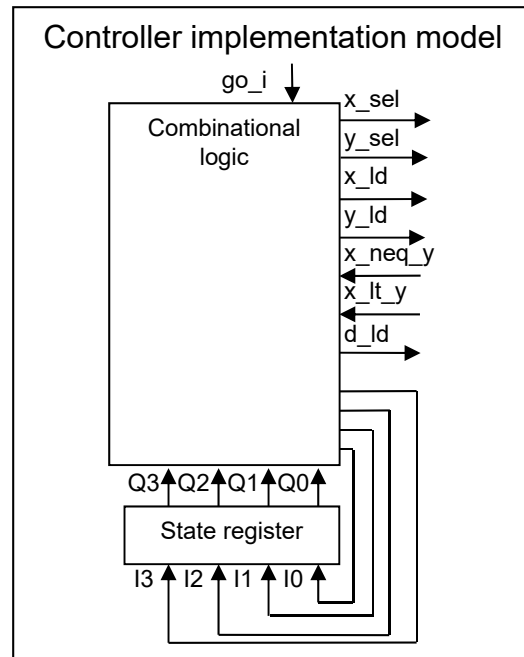

Controller state table for the GCD example


16

Inputs							Outputs								
Q3	Q2	Q1	Q0	x_ne q_y	x_lt_ y	go_i	I3	I2	I1	I0	x_sel	y_sel	x_ld	y_ld	d_ld
0	0	0	0	*	*	*	0	0	0	1	X	X	0	0	0
0	0	0	1	*	*	0	0	0	1	0	X	X	0	0	0
0	0	0	1	*	*	1	0	0	1	1	X	X	0	0	0
0	0	1	0	*	*	*	0	0	0	1	X	X	0	0	0
0	0	1	1	*	*	*	0	1	0	0	0	X	1	0	0
0	1	0	0	*	*	*	0	1	0	1	X	0	0	1	0
0	1	0	1	0	*	*	1	0	1	1	X	X	0	0	0
0	1	0	1	1	*	*	0	1	1	0	X	X	0	0	0
0	1	1	0	*	0	*	1	0	0	0	X	X	0	0	0
0	1	1	0	*	1	*	0	1	1	1	X	X	0	0	0
0	1	1	1	*	*	*	1	0	0	1	X	1	0	1	0
1	0	0	0	*	*	*	1	0	0	1	1	X	1	0	0
1	0	0	1	*	*	*	1	0	1	0	X	X	0	0	0
1	0	1	0	*	*	*	0	1	0	1	X	X	0	0	0
1	0	1	1	*	*	*	1	1	0	0	X	X	0	0	1
1	1	0	0	*	*	*	0	0	0	0	X	X	0	0	0
1	1	0	1	*	*	*	0	0	0	0	X	X	0	0	0
1	1	1	0	*	*	*	0	0	0	0	X	X	0	0	0
1	1	1	1	*	*	*	0	0	0	0	X	X	0	0	0

Completing the GCD custom single-purpose processor design

17

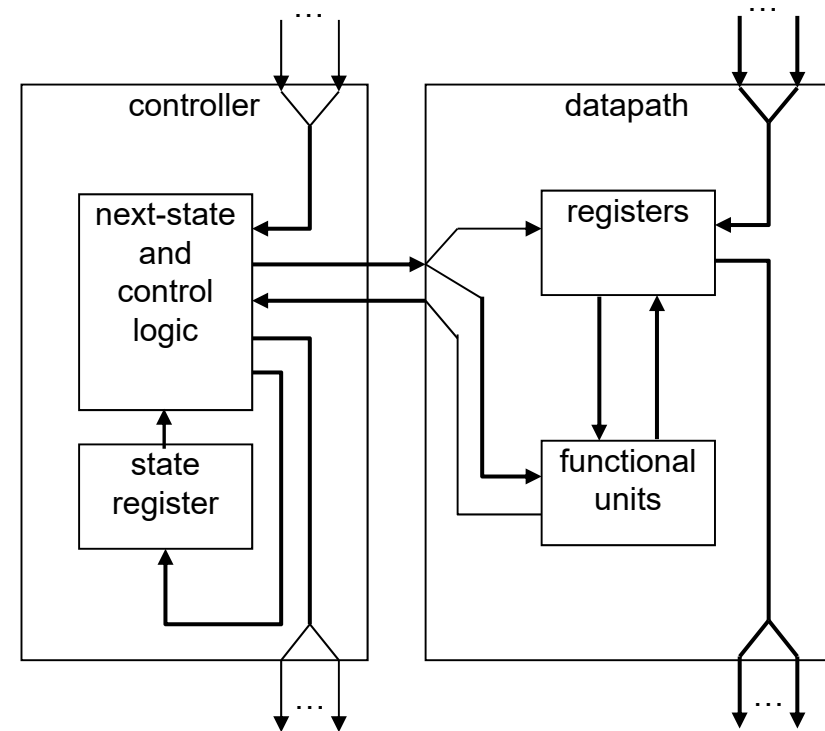- We finished the datapath
- We have a state table for the next state and control logic
 - ▣ All that's left is combinational logic design
- This is *not* an optimized design, but we see the basic steps





a view inside the controller and datapath

RT-level custom single-purpose processor design

18


- We often start with a state machine
 - ▣ Rather than algorithm
 - ▣ Cycle timing often too central to functionality
- Example
 - ▣ Bus bridge that converts 4-bit bus to 8-bit bus
 - ▣ Start with FSMD
 - ▣ Known as register-transfer (RT) level
 - ▣ Exercise: complete the design

Problem Specification

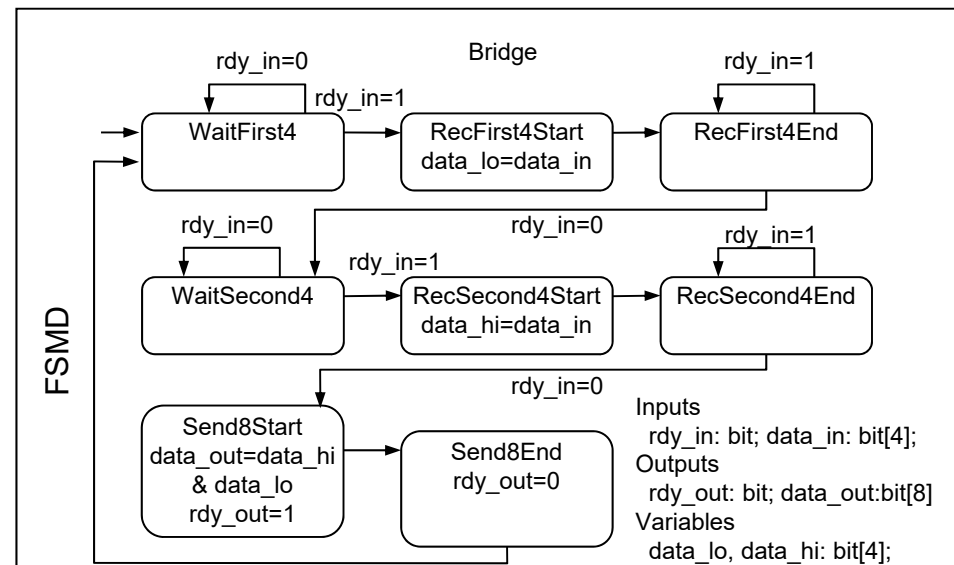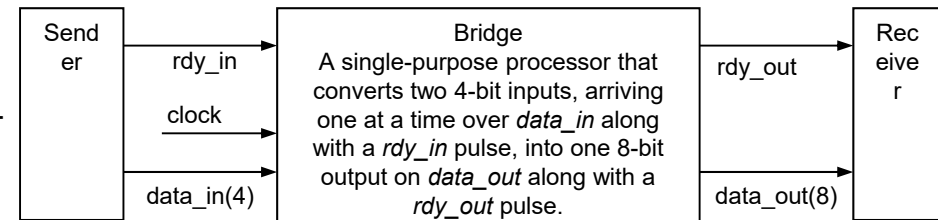

RT-level custom single-purpose processor design (cont')

19

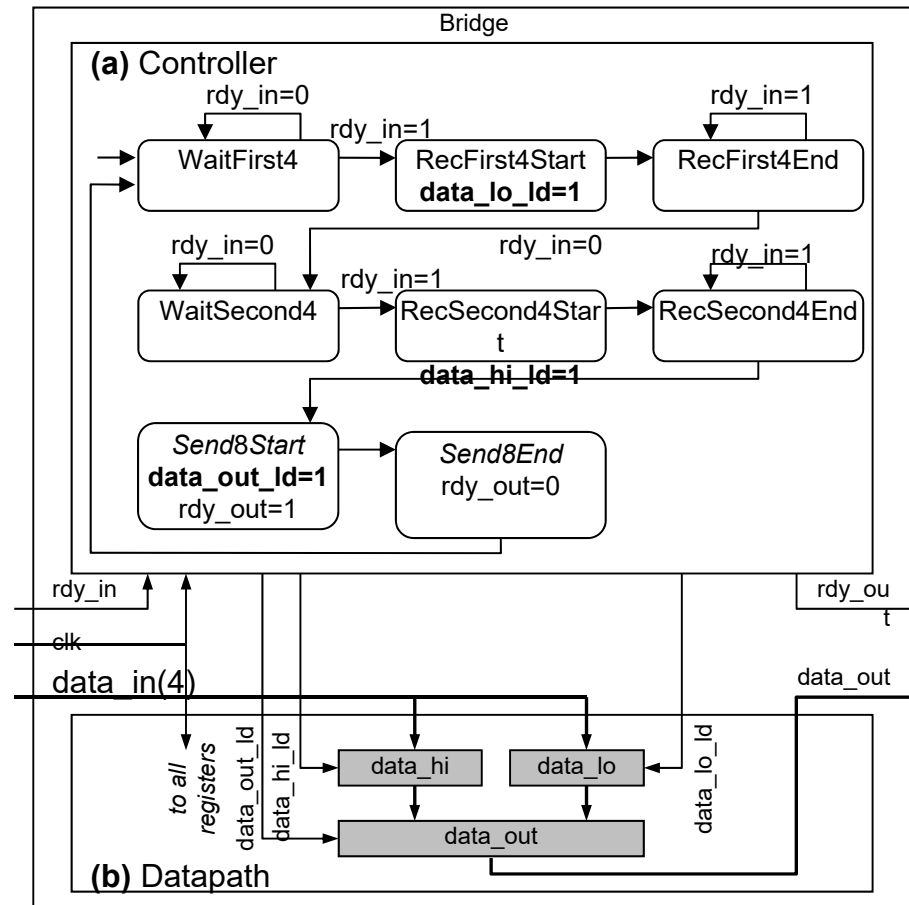

Optimizing single-purpose processors

20

- Optimization is the task of making design metric values the best possible
- Optimization opportunities
 - ▣ original program
 - ▣ FSMD
 - ▣ datapath
 - ▣ FSM

Optimizing the original program

21

- Analyze program attributes and look for areas of possible improvement
 - ▣ number of computations
 - ▣ size of variable
 - ▣ time and space complexity
 - ▣ operations used
 - multiplication and division very expensive

Optimizing the original program (cont')

22

original program

```
0: int x, y;  
1: while (1) {  
2:   while (!go_i);  
3:   x = x_i;  
4:   y = y_i;  
5:   while (x != y) {  
6:     if (x < y)  
7:       y = y - x;  
8:     else  
9:       x = x - y;  
9:   }  
9:   d_o = x;  
}
```

replace the subtraction
operation(s) with modulo
operation in order to
speed up program

optimized program

```
0: int x, y, r;  
1: while (1) {  
2:   while (!go_i);  
   // x must be the larger number  
3:   if (x_i >= y_i) {  
4:     x=x_i;  
5:     y=y_i;  
   }  
6:   else {  
7:     x=y_i;  
8:     y=x_i;  
   }  
9:   while (y != 0) {  
10:    r = x % y;  
11:    x = y;  
12:    y = r;  
   }  
13:   d_o = x;  
}
```

GCD(42, 8) - 9 iterations to complete the loop
x and y values evaluated as follows : (42, 8), (43,
8), (26,8), (18,8), (10, 8), (2,8), (2,6), (2,4), (2,2).

GCD(42,8) - 3 iterations to complete the loop
x and y values evaluated as follows: (42, 8),
(8,2), (2,0)


Optimizing the FSMD

23

- Areas of possible improvements
 - ▣ merge states
 - states with constants on transitions can be eliminated, transition taken is already known
 - states with independent operations can be merged
 - ▣ separate states
 - states which require complex operations ($a*b*c*d$) can be broken into smaller states to reduce hardware size
 - ▣ scheduling

Optimizing the FSMD (cont.)

24

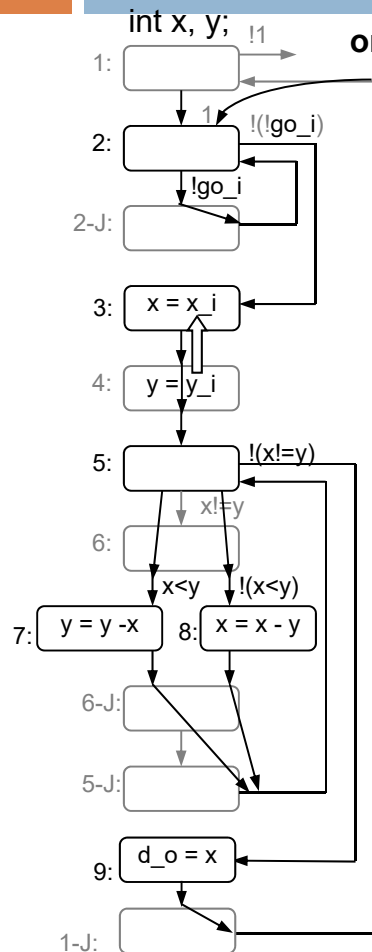

original FSMD

eliminate state 1 – transitions have constant values

merge state 2 and state 2J – no loop operation in between them


merge state 3 and state 4 – assignment operations are independent of one another

merge state 5 and state 6 – transitions from state 6 can be done in state 5

eliminate state 5J and 6J – transitions from each state can be done from state 7 and state 8, respectively

eliminate state 1-J – transition from state 1-J can be done directly from state 9

optimized FSMD

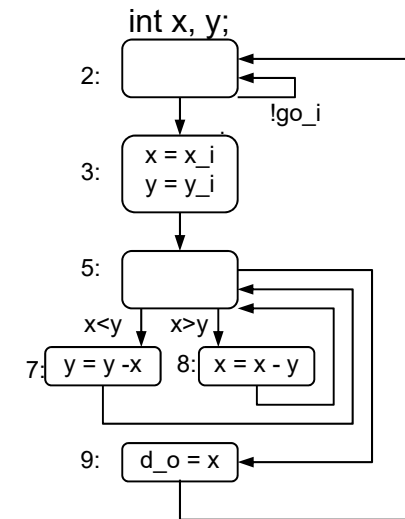

Optimizing the datapath

25

- Sharing of functional units
 - ▣ one-to-one mapping, as done previously, is not necessary
 - ▣ if same operation occurs in different states, they can share a single functional unit
- Multi-functional units
 - ▣ ALUs support a variety of operations, it can be shared among operations occurring in different states

Optimizing the FSM

26

□ State encoding

- ▣ task of assigning a unique bit pattern to each state in an FSM
- ▣ size of state register and combinational logic vary
- ▣ can be treated as an ordering problem

□ State minimization

- ▣ task of merging equivalent states into a single state
 - state equivalent if for all possible input combinations the two states generate the same outputs and transitions to the next same state


27

Peripherals

Timers, counters, watchdog timers

28


- Timer: measures time intervals
 - ▣ To generate timed output events
 - e.g., hold traffic light green for 10 s
 - ▣ To measure input events
 - e.g., measure a car's speed
- Based on counting clock pulses
 - E.g., let Clk period be 10 ns
 - And we count 20,000 Clk pulses
 - Then 200 microseconds have passed
 - 16-bit counter would count up to $65,535 \times 10 \text{ ns} = 655.35 \text{ microsec.}$, resolution = 10 ns
 - Top: indicates top count reached, wrap-around

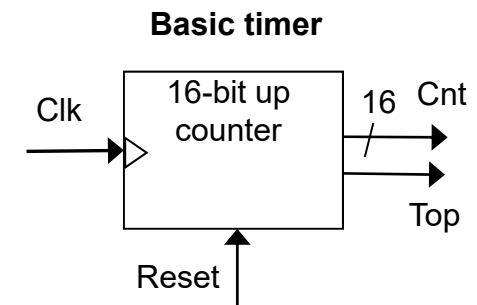

Counters

29

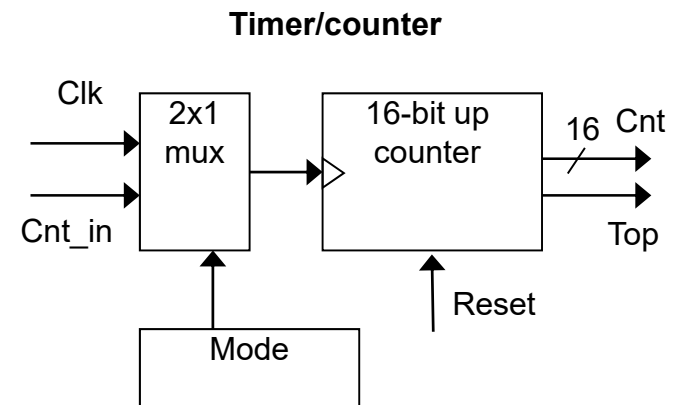- Counter: like a timer, but counts pulses on a general input signal rather than clock
 - ▣ e.g., count cars passing over a sensor
 - ▣ Can often configure device as either a timer or counter



Other timer structures

30


Interval timer

- Indicates when desired time interval has passed
- We set terminal count to desired interval
 - $\text{Number of clock cycles} = \text{Desired time interval} / \text{Clock period}$

Cascaded counters


Prescaler

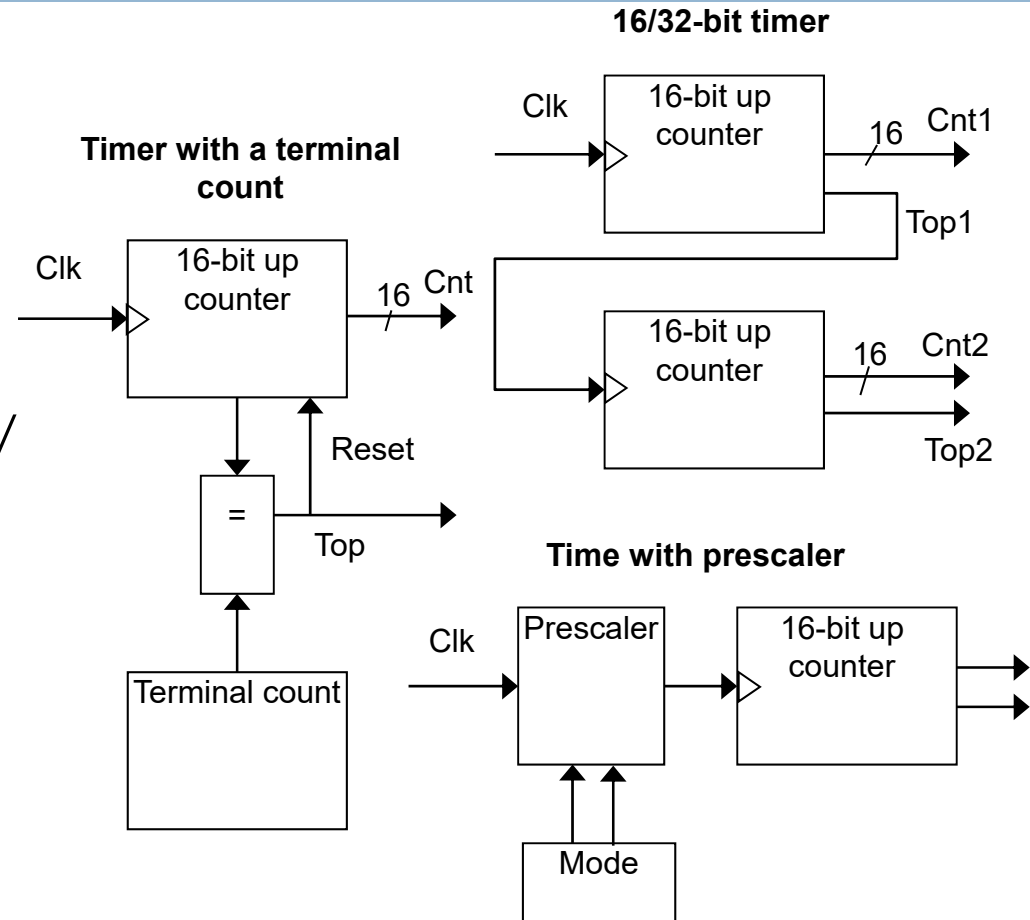- Divides clock
- Increases range, decreases resolution



Example: Reaction Timer

31

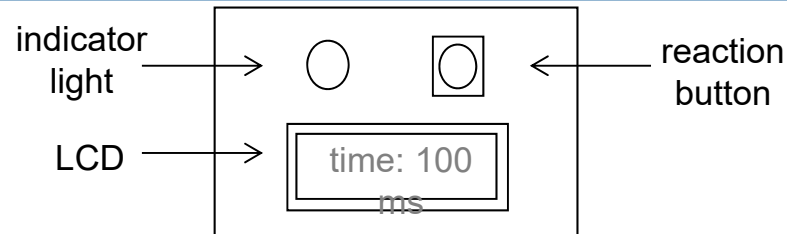

- Measure time between turning light on and user pushing button
 - ▣ 16-bit timer, clk period is 83.33 ns, counter increments every 6 cycles
 - ▣ Resolution = $6 \times 83.33 = 0.5$ microsec.
 - ▣ Range = 65535×0.5 microseconds = 32.77 milliseconds
 - ▣ Want program to count millisec., so initialize counter to $65535 - 1000 / 0.5 = 63535$

```
/* main.c */

#define MS_INIT    63535
void main(void){
    int count_milliseconds = 0;

    configure timer mode
    set Cnt to MS_INIT


    wait a random amount of time
    turn on indicator light
    start timer

    while (user has not pushed reaction button){
        if(Top) {
            stop timer
            set Cnt to MS_INIT
            start timer
            reset Top
            count_milliseconds++;
        }
    }
    turn light off
    printf("time: %i ms", count_milliseconds);
}
```

Watchdog timer

32

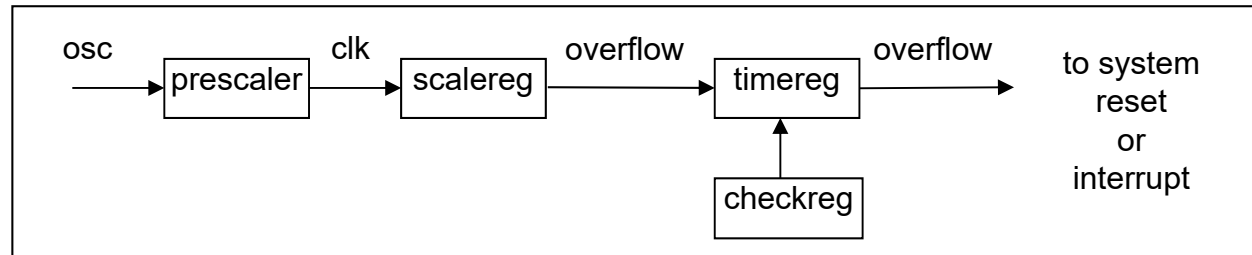- Must reset timer every X time unit, else timer generates a signal
- Common use: detect failure, self-reset
- Another use: timeouts
 - ▣ e.g., ATM machine
 - ▣ 16-bit timer, 2 microsec. resolution
 - ▣ $\text{timereg value} = 2 \times (2^{16} - 1) - X = 131070 - X$
 - ▣ For 2 min., $X = 120,000$ microsec.



```
/* main.c */  
  
main(){  
    wait until card inserted  
    call watchdog_reset_routine  
  
    while(transaction in progress){  
        if(button pressed){  
            perform corresponding action  
            call watchdog_reset_routine  
        }  
    }  
  
    /* if watchdog_reset_routine not called  
    every < 2 minutes,  
    interrupt_service_routine is called */  
}
```

```
watchdog_reset_routine(){  
    /* checkreg is set so we can load value  
    into timereg. Zero is loaded into  
    scalereg and 11070 is loaded into  
    timereg */  
  
    checkreg = 1  
    scalereg = 0  
    timereg = 11070  
}  
  
void interrupt_service_routine(){  
    eject card  
    reset screen  
}
```


Serial Transmission Using UARTs

33

- UART: Universal Asynchronous Receiver Transmitter
 - ▣ Takes parallel data and transmits serially
 - ▣ Receives serial data and converts to parallel
- Parity: extra bit for simple error checking
- Start bit, stop bit
- Baud rate
 - ▣ signal changes per second
 - ▣ bit rate usually higher

