



#### **Outline**

- Problem 1 cache
  - Specification
  - Verification
- Problem 2 booting
  - Specification
  - → Verification
- Submission rule





# Problem 1 - cache


Specification








### **System Architecture**

 





### Specification(1/7)

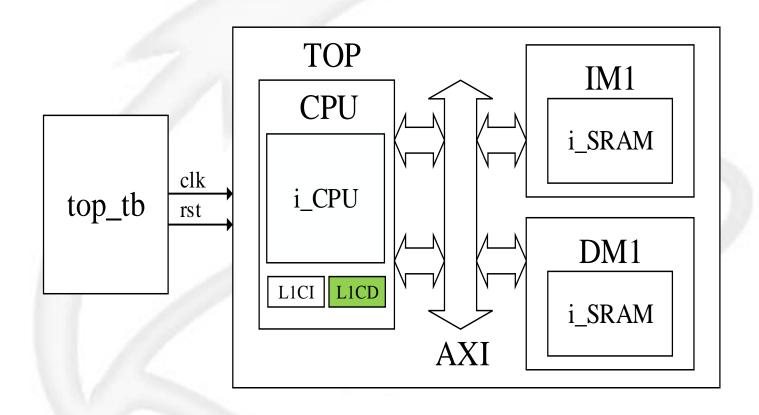





## Specification(2/7)

I	clk	input	1	clock
	rst	input	1	reset (active high)
	core_addr	input	32	address from CPU
	core_req	input	1	memory access request from CPU
	core_write	input	1	write signal from CPU
	core_in	input	32	data from CPU
	core_type	input	3	write/read byte, half word, or word (listed in include/def.svh) from CPU
	D_out	input	32	data from CPU wrapper
	D_wait	input	1	wait signal from CPU wrapper
	core_out	output	32	data to CPU
	core_wait	output	1	wait signal to CPU
L1C_data	D_req	output	1	request to CPU wrapper
	D_addr	output	32	address to CPU wrapper
	D_write	output	1	write signal to CPU wrapper
	D_in	output	32	write data to CPU wrapper
	D_type	output	3	write/read byte, half word, or word (listed in include/def.svh) to CPU wrapper
	valid	logic	64	valid bits of each cache line
	index	logic	6	address to tag array/data array
	TA_write	logic	1	write signal to tag_array
	TA_read	logic	1	read signal to tag_array
	TA_in	logic	22	write data to tag_array
10.75	TA_out	logic	22	read data from tag_array
	DA_write	logic	16	write signal to data_array
	DA_read	logic	1	read signal to data_array
	DA_in	logic	128	write data to data_array
	DA_out	logic	128	read data from data_array


Inputs and outputs of module L1C\_data/L1C\_inst has declared in src/L1C\_data.sv and src/L1C\_inst.sv. You can modify input and output bit width if needed.







### Specification(3/7)

 





### Specification(4/7)

	clk	input	1	clock	
	rst	input	1	reset (active high)	
	core_addr	input	32	address from CPU	
	core_req	input	1	memory access request from CPU	
	core_write	input	1	write signal from CPU	
	core_in	input	32	data from CPU	
	core_type	input	3	write/read byte, half word, or word (listed in include/def.svh) from CPU	
	I_out	input	32	data from CPU wrapper	
	I_wait	input	1	wait signal from CPU wrapper	
	core_out	output	32	data to CPU	
- 0	core_wait	output	1	wait signal to CPU	
L1C_inst	I_req	output	1	request to CPU wrapper	
	I_addr	output	32	address to CPU wrapper	
1.7	I_write	output	1	write signal to CPU wrapper	
	I_in	output	32	write data to CPU wrapper	
	I_type	output	3	write/read byte, half word, or word (listed in include/def.svh) to CPU wrapper	
	valid	logic	64	valid bits of each cache line	
	index	logic	6	address to tag array/data array	
	TA_write	logic	1	write signal to tag_array	
	TA_read	logic	1	read signal to tag_array	
10.00	TA_in	logic	22	write data to tag_array	
10000	TA_out	logic	22	read data from tag_array	
	DA_write	logic	16	write signal to data_array	
	DA_read	logic	1	read signal to data_array	
	DA_in	logic	128	write data to data_array	
	DA_out	logic	128	read data from data_array	

Inputs and outputs of module L1C\_data/L1C\_inst has declared in src/L1C\_data.sv and src/L1C\_inst.sv. You can modify input and output bit width if needed.




### Specification(5/7)

Table 1-1: Cache actions on different condition

condition	core read	core write
hit	transmit data into core	write data into cache and memory
miss	read a line from memory	only write data into memory

Table 1-2: Array characteristics

Type	Lines	Words per line	Bytes per word	Bits per line	Writing mode
data_array	64	4	4	128	Byte Write
tag_array	04	1		22	Word Write

 


Hit = valid && (TA\_out equal core\_addr[31:10])




 
### Specification(6/7)

Tag\_array is word write, while data\_array is byte write







### Specification(7/7)

Table 1-2: Caches specification₽

Type₽	Size₽	Line Bits₽	Associativity₽	Write Policy₽	
Cache₽	1 KB₽ 128	120 -	Direct Map₽	Hit₽	write through₽
		128₽		miss₽	write around∂

condition	core read₽	core write₽	
hit₄□	transmit data into core₽	write data into cache and memory	
miss₽	read a line from memory₽	only write data into memory₽	





# Problem 1 - cache

Verification







#### **Report Requirements**

- Proper explanation of your design is required for full credits.
- □ Block diagrams shall be drawn to depict your designs.
- □ Show the result of JasperGold with full prove, explain the assertion you modified.
- □ Show the hit rate of your instruction cache and data cache
- □ Show the IPC (instruction per cycle) of your CPU

cache hit rate 
$$= \frac{Number\ of\ cache\ hits}{Number\ of\ cache\ hits\ +\ Number\ of\ cache\ misses}$$

$$IPC = \frac{Number\ of\ instructions\ CPU\ execute}{Total\ cycles}$$





# Problem 2 - booting

**Specification** 





### **Slave Configuration**

#### **Table 1-5: Slave configuration**

NAME	Number	Start address	End address	
ROM	ROM Slave 0		0x0000_1FFF	
IM	Slave 1	0x0001_0000	0x0001_FFFF	
DM	Slave 2	0x0002_0000	0x0002_FFFF	
sensor_ctrl	Slave 3	0x1000_0000	0x1000_03FF	
DRAM	Slave 4	0x2000_0000	0x201F_FFFF	

You should design all slave wrappers (except slave 3) !!





### ROM

	System signals					
CK	input	1	System clock			
		Memory	ports			
DO	output	32	ROM data output			
OE	input	1	Output enable (active high)			
CS	input	1	Chip select (active high)			
A input		12	ROM address input			
		Memory	Space			
Memory_byte0	reg	8	Size: [0:4095]			
Memory_byte1	reg	8	Size: [0:4095]			
Memory_byte2	reg	8	Size: [0:4095]			
Memory_byte3	reg	8	Size: [0:4095]			

ROM







#### **DRAM**


	System signals					
	CK	input	1	System clock		
	RST	input	1	System reset (active high)		
			Memory	ports		
	CSn	innut	1	DRAM Chip Select		
	CSII	input	1	(active low)		
	WEn	input	4	DRAM Write Enable		
1	VVIZII	при	7	(active low)		
	RASn	input	1	DRAM Row Access Strobe		
	KASII	при	1	(active low)		
DRAM	CASn	input	1	DRAM Column Access Strobe		
				(active low)		
	A	input	11	DRAM Address input		
	D	input	32	DRAM data input		
	Q	output	32	DRAM data output		
	VALID	output	1	DRAM data output valid		
		Memory		space		
	Memory_byte0	reg	8	Size: [0:2097151]		
1//	Memory_byte1	reg	8	Size: [0:2097151]		
	Memory_byte2	reg	8	Size: [0:2097151]		
	Memory_byte3	reg	8	Size: [0:2097151]		

- ★ Row address is 11-bit and column address is 10-bit
- ★ Row addr = araddr/awaddr [22:12]
- ★ Col addr = araddr/awaddr[11:2]





### **System Architecture**

 





# Problem 2 - booting

Verification



### **Verification(1/7)**

- prog0
  - → 測試45個instruction (助教提供)
- prog1
  - Sort algorithm of half-word
- prog2
  - Gray scale
- prog3
  - Matrix multiplication



### **Verification (2/7)**

- Booting
  - → The booting program is stored in ROM
  - Moves data from DRAM to IM and DM


```
extern unsigned int dram i start;
extern unsigned int dram i end;
extern unsigned int imem start;
extern unsigned int
                     sdata start;
extern unsigned int
                     sdata end;
extern unsigned int
                     sdata paddr start;
extern unsigned int
                     data start;
extern unsigned int
                     data end;
extern unsigned int
                     data paddr start;
```



# LPHPLMB VLSI Design LAB
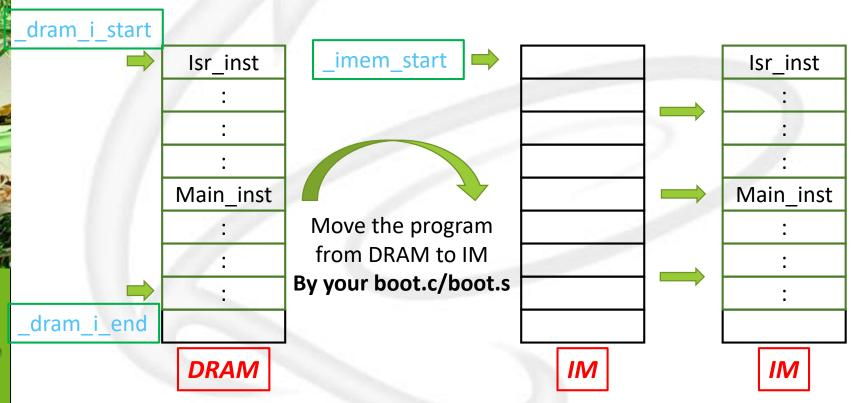
### Verification (3/7)

- \_dram\_i\_start = instruction start address in DRAM.
- \_dram\_i\_end = instruction end address in DRAM.
- \_\_imem\_start = instruction start address in IM







 
### Verification (4/7)

- \_data\_start = Main\_data start address in DM.
- \_data\_end = Main\_data end address in DM.
- \_\_data\_paddr\_start = Main\_data start address in DRAM







 
### **Verification (5/7)**

- \_sdata\_start = Main\_data start address in DM.
- \_sdata\_end = Main\_data end address in DM.
- \_\_sdata\_paddr\_start = Main\_data start address in DRAM





### **Verification(6/7)**



12

1f

25

12

**1**f

25

Header (54 bytes) x = 0.11\*b + 0.59\*g + 0.3\*r= 0.11\*25 + 0.59\*1f + 0.3\*12

y = 0.11\*b + 0.59\*g + 0.3\*r= 0.11\*25 + 0.59\*1f + 0.3\*12

binary image bmp start M Size of BMP file (byte)

(54 bytes) The number of bits per pixel

X

Header


Address a b Dump 偏移的byte數 00 (18) 00 00 00 00 00 00 0e 00 00<u>c4 %e 00 00 00</u> \$.?..?.... 00000024 00000030 00 00 00 00 00 25 1f 12 0000003c 25 1f 12 8..8..8..8.. 00000048 25 1f 12 25 1f 12 25 1f 12 25 1f 12 %..%..%.. 00000054 25 1f 12 25 1f 12 25 1f 12 25 1f 12 8..%..%.. 00000060 25 1f 12 25 1f 12 25 1f 12 25 1f 12 0000006c 25 1f 12 25 1f 12 25 1f 12 25 1f 12 00000078 25 1

BMP檔案解析參考資料:



### **Verification(7/7)**

Matrix Multiplication

 

$$\begin{pmatrix} \textit{data} \cdot 1 & \textit{data} \cdot 2 & \textit{data} \cdot 3 \\ \textit{data} \cdot 4 & \textit{data} \cdot 5 & \textit{data} \cdot 6 \end{pmatrix} \cdot \begin{pmatrix} \textit{data} \cdot 7 & \textit{data} \cdot 8 & \textit{data} \cdot 9 & \textit{data} \cdot 10 \\ \textit{data} \cdot 11 & \textit{data} \cdot 12 & \textit{data} \cdot 13 & \textit{data} \cdot 14 \\ \textit{data} \cdot 15 & \textit{data} \cdot 16 & \textit{data} \cdot 17 & \textit{data} \cdot 18 \end{pmatrix} = \begin{pmatrix} \textit{result} \cdot 1 & \textit{result} \cdot 2 & \textit{result} \cdot 3 & \textit{result} \cdot 3 \\ \textit{result} \cdot 5 & \textit{result} \cdot 6 & \textit{result} \cdot 7 & \textit{result} \cdot 8 \end{pmatrix}$$





### **Report Requirements**

- Proper explanation of your design is required for full credits.
- Block diagrams shall be drawn to depict your designs.
- Show your screenshots of the waveforms and the simulation results on the terminal for the different test cases in your report and illustrate the correctness of your results. Explain cache read hit/read miss/write hit/write miss with waveform.
- Explain your codes of program1, program2 and program3.
- Explain your codes of boot.c.
- □ Report the number of lines of your RTL code, the final results of running Superlint and 3~5 most frequent warning/errors in your code. Describe how you modify your code to comply with Superlint.





### **Report Requirements**

Report and show screenshots of your prog0 to prog3 simulation time after synthesis and total cell area of your design.





### **Submission rule**





- □ 請使用附在檔案內的Submission Cover
- □ 請勿將code貼在.docx內 (program的程式可截圖 說明)
  - → 請將.sv包在壓縮檔內,不可截圖於.docx中
- 需要Summary及Lessons learned(Summary table請放在第二頁,清楚列出有完成以及沒完成的部分)
- □ 若兩人為一組,須寫出貢獻度(貢獻度請放第二 頁)
  - Ex: A(N26071234) 55%, B(N26075678) 45%
  - → Total 100%
  - → 自己一組則不用寫





### **Specification**

□ Module name須符合下表要求

	Name				
Category	File	Module	Instance		
RTL	top.sv	top	TOP		
Gate-Level	top_syn.v	top	TOP		
RTL	L1C_inst.sv	L1C_inst	L1CI		
RTL	L1C_data.sv	L1C_data	L1CD		
RTL	SRAM_wrapper.sv	SRAM_wrapper	IM1		
RTL	SRAM_wrapper.sv	SRAM_wrapper	DM1		
RTL	SRAM_rtl.sv	SRAM	i_SRAM		
RTL	tag_array_wrapper.sv	tag_array_wrapper	TA		
RTL	tag_array_rtl.sv	tag_array	i_tag_array		
RTL	data_array_wrapper.sv	data_array_wrapper	DA		
RTL	RTL data_array_rtl.sv		i_data_array		
Behavior	ROM.v	ROM	i_ROM		
Behavior	DRAM.v	DRAM	i_DRAM		

□ 需按照要求命名,以免testbench抓不到正確的名稱

## 繳交檔案 (1/2)

- □ 依照檔案結構壓縮成 ".tar" 格式
  - → 在Homework主資料夾(N260XXXXX)使用make tar產生的tar檔即可符合要求
- □ 檔案結構請依照作業說明
- □ 請勿附上檔案結構內未要求繳交的檔案
  - → 在Homework主資料夾(N260XXXXX)使用make clean即可刪除不必要的檔案
- □ 請務必確認繳交檔案可以在SoC實驗室的工作站下compile,且功能正常
- □ 無法compile將直接以0分計算
- □ 請勿使用generator產生code再修改
- □ 禁止抄襲





- □ 一組只需一個人上傳作業到Moodle
  - → 兩人以上都上傳會斟酌扣分
- □ 壓縮檔、主資料夾名稱、Report名稱、StudentID 檔案內的學號都要為上傳者的學號,其他人則在 Submission Cover內寫上自己的學號。
  - → Ex: A(N26101234)負責上傳,組員為B(N26105678)
  - → N26101234.tar (壓縮檔) N26101234 (主資料夾) N26101234.docx (Report, Cover寫上兩者的學號)





### 繳交期限

- □ 2022/11/30 (三) 14:00前上傳
  - → 不接受遲交,請務必注意時間
  - → Moodle只會留存你最後一次上傳的檔案,檔名只要是「N260XXXXX.tar」即可,不需要加上版本號





# Thanks for your participation and attendance!!



