

# Homework I 說明

Instructor : Lih-Yih Chiou

TA : Vivian

Date : 09/07/2022



# Outline


- 作業內容說明
- 作業驗證說明
- 作業繳交注意事項



# 作業内容説明

# Problem 1

- 根據作業中附的RISC-V ISA，完成一個pipelined CPU

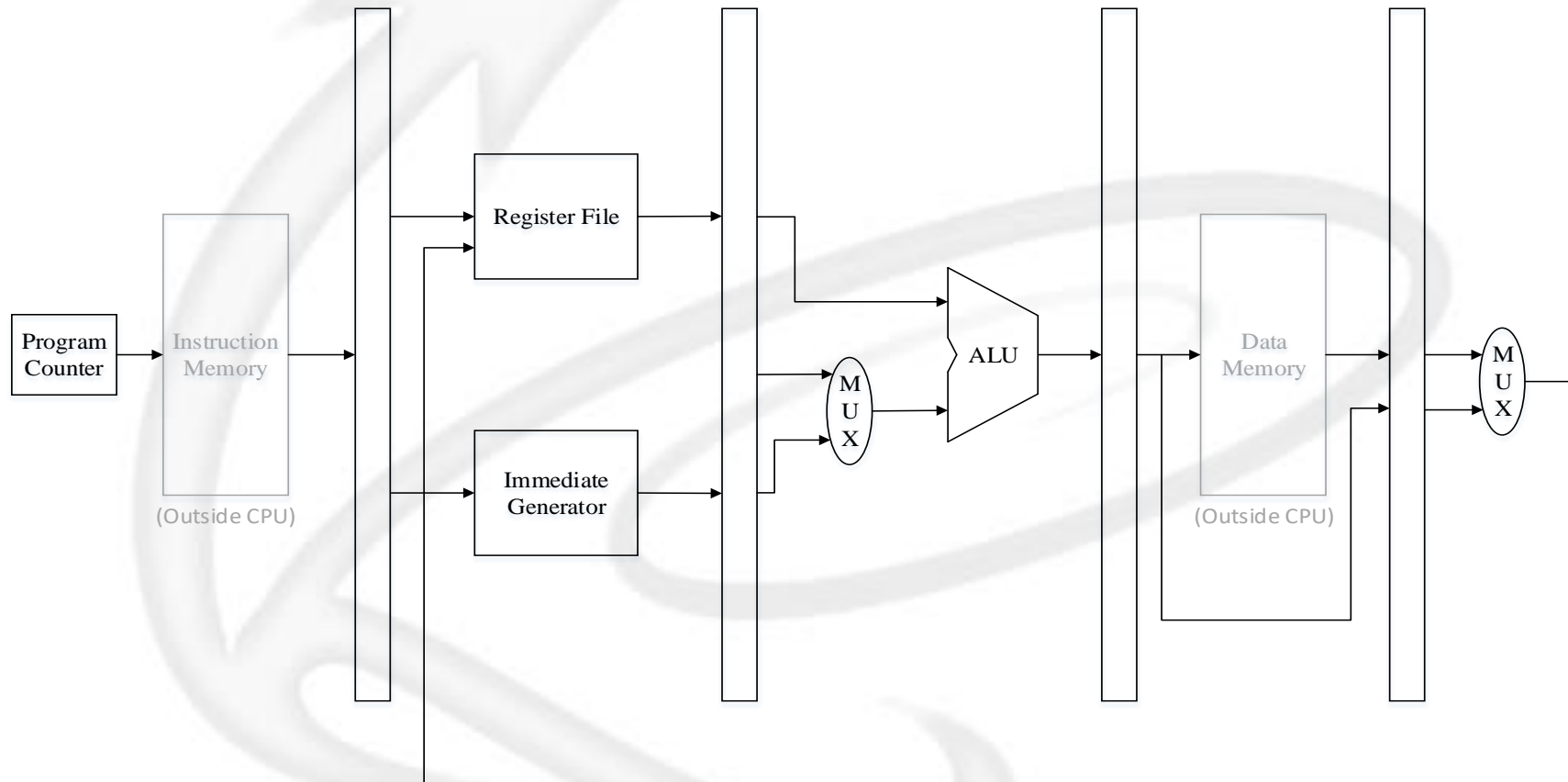



# Problem 1 Specification

- ❑ Implement the 41 instructions as listed. The number of pipeline stage is 5.
- ❑ Register File size: 32x32-bit  
→ x0 is read only 0.
- ❑ Instruction memory size: 16Kx32-bit
- ❑ Data memory size: 16Kx32-bit
- ❑ Timescale: 1ns/10ps
- ❑ Maximum Clock period: 20ns (50MHz)
- ❑ Control and Status Register: 2x64-bit

# Problem 1 – Instructions (1/4)

## R-type

31	25	24	20	19	15	14	12	11	7	6	0		
funct7		rs2		rs1		funct3		rd		opcode		Mnemonic	Description
0000000		rs2		rs1		000		rd		0110011		ADD	rd = rs1 + rs2
0100000		rs2		rs1		000		rd		0110011		SUB	rd = rs1 - rs2
0000000		rs2		rs1		001		rd		0110011		SLL	rd = rs1 <sub>u</sub> << rs2[4:0]
0000000		rs2		rs1		010		rd		0110011		SLT	rd = (rs1 <sub>s</sub> < rs2 <sub>s</sub> )? 1:0
0000000		rs2		rs1		011		rd		0110011		SLTU	rd = (rs1 <sub>u</sub> < rs2 <sub>u</sub> )? 1:0
0000000		rs2		rs1		100		rd		0110011		XOR	rd = rs1 <sub>u</sub> ^ rs2
0000000		rs2		rs1		101		rd		0110011		SRL	rd = rs1 <sub>u</sub> >> rs2[4:0]
0100000		rs2		rs1		101		rd		0110011		SRA	rd = rs1 <sub>s</sub> >> rs2[4:0]
0000000		rs2		rs1		110		rd		0110011		OR	rd = rs1   rs2
0000000		rs2		rs1		111		rd		0110011		AND	rd = rs1 & rs2

## I-type

31	20	19	15	14	12	11	7	6	0		
imm[11:0]		rs1		funct3		rd		opcode		Mnemonic	Description
imm[11:0]		rs1		010		rd		0000011		LW	$rd = M[rs1+imm]$
imm[11:0]		rs1		000		rd		0010011		ADDI	$rd = rs1 + imm$
imm[11:0]		rs1		010		rd		0010011		SLTI	$rd = (rs1_s < imm_s)? 1:0$
imm[11:0]		rs1		011		rd		0010011		SLTIU	$rd = (rs1_u < imm_u)? 1:0$
imm[11:0]		rs1		100		rd		0010011		XORI	$rd = rs1 \wedge imm$
imm[11:0]		rs1		110		rd		0010011		ORI	$rd = rs1 \mid imm$
imm[11:0]		rs1		111		rd		0010011		ANDI	$rd = rs1 \& imm$
imm[11:0]		rs1		000		rd		0000011		LB	$rd = M[rs1+imm]_{bs}$
0000000	shamt	rs1		001		rd		0010011		SLLI	$rd = rs1_u \ll shamt$
0000000	shamt	rs1		101		rd		0010011		SRLI	$rd = rs1_u \gg shamt$
0100000	shamt	rs1		101		rd		0010011		SRAI	$rd = rs1_s \gg shamt$
imm[11:0]		rs1		000		rd		1100111		JALR	$rd = PC + 4$ $PC = imm + rs1$ (Set LSB of PC to 0)
imm[11:0]		rs1		001		rd		0000011		LH	$rd = M[rs1+imm]_{hs}$
imm[11:0]		rs1		100		rd		0000011		LHU	$rd = M[rs1+imm]_{hu}$
imm[11:0]		rs1		101		rd		0000011		LBU	$rd = M[rs1+imm]_{bu}$

# Problem 1 – Instructions (2/4)

## □ S-type

31	25	24	20	19	15	14	12	11	7	6	0		
imm[11:5]		rs2		rs1		funct3		imm[4:0]		opcode		Mnemonic	Description
imm[11:5]		rs2		rs1		010		imm[4:0]		0100011		SW	$M[rs1+imm] = rs2$
imm[11:5]		rs2		rs1		000		imm[4:0]		0100011		SB	$M[rs1+imm]_b = rs2_b$
imm[11:5]		rs2		rs1		001		imm[4:0]		0100011		SH	$M[rs1+imm]_h = rs2_h$

## □ B-type

31	25	24	20	19	15	14	12	11	7	6	0		
imm[12 10:5]		rs2		rs1		funct3		imm[4:1 11]		opcode		Mnemonic	Description
imm[12 10:5]		rs2		rs1		000		imm[4:1 11]		1100011		BEQ	PC = (rs1 == rs2)? PC + imm: PC + 4
imm[12 10:5]		rs2		rs1		001		imm[4:1 11]		1100011		BNE	PC = (rs1 != rs2)? PC + imm: PC + 4
imm[12 10:5]		rs2		rs1		100		imm[4:1 11]		1100011		BLT	PC = (rs1 <sub>s</sub> < rs2 <sub>s</sub> )? PC + imm: PC + 4
imm[12 10:5]		rs2		rs1		101		imm[4:1 11]		1100011		BGE	PC = (rs1 <sub>s</sub> ≥ rs2 <sub>s</sub> )? PC + imm: PC + 4
imm[12 10:5]		rs2		rs1		110		imm[4:1 11]		1100011		BLTU	PC = (rs1 <sub>u</sub> < rs2 <sub>u</sub> )? PC + imm: PC + 4
imm[12 10:5]		rs2		rs1		111		imm[4:1 11]		1100011		BGEU	PC = (rs1 <sub>u</sub> ≥ rs2 <sub>u</sub> )? PC + imm: PC + 4

## □ U-type

31	12	11	7	6	0		
imm[31:12]		rd		opcode		Mnemonic	Description
imm[31:12]		rd		0010111		AUIPC	rd = PC + imm
imm[31:12]		rd		0110111		LUI	rd = imm

## □ J-type

31	12	11	7	6	0		
imm[20 10:1 11 19:12]		rd		opcode		Mnemonic	Description
imm[20 10:1 11 19:12]		rd		1101111		JAL	rd = PC + 4 PC = PC + imm

# Problem 1 – Instructions (3/4)

## Control and Status Register (CSR) instructions

31	20	19	15	14	12	11	7	6	0		
imm[11:0]		rs1		funct3		rd		opcode		Mnemonic	Description
csr		rs1		001		rd		1110011		CSRRW	rd = csr, if #rd != 0 csr = rs1
csr		rs1		010		rd		1110011		CSRRS	rd = csr, if #rd != 0 csr = csr   rs1, if that csr bit is writable and #rs1 != 0
csr		rs1		011		rd		1110011		CSRRC	rd = csr, if #rd != 0 csr = csr & (~rs1), if that csr bit is writable and #rs1 != 0
csr		uimm[4:0]		101		rd		1110011		CSRRWI	rd = csr, if #rd != 0 csr = uimm(zero-extend)
csr		uimm[4:0]		110		rd		1110011		CSRRSI	rd = csr, if #rd != 0 csr = csr   uimm(zero-extend), if that csr bit is writable and uimm != 0
csr		uimm[4:0]		111		rd		1110011		CSRRCI	rd = csr, if #rd != 0 csr = csr & (~uimm(zero- extend)), if that csr bit is writable and uimm != 0

31	20	19	15	14	12	11	7	6	0		
imm[11:0]		rs1		funct3		rd		opcode		Mnemonic	Description
110010000010		00000		010		rd		1110011		RDINSTRETH	rd = instret[63:32]
110000000010		00000		010		rd		1110011		RDINSTRET	rd = instret [31:0]
110010000000		00000		010		rd		1110011		RDCYCLEH	rd = cycle[63:32]
110000000000		00000		010		rd		1110011		RDCYCLE	rd = cycle[31:0]




# Problem 1 – Instructions (4/4)

## Control and Status Register (CSR) instructions

### → RDINSTRET/RDINSTRETH

- ◆ Read CSR instret , which is the CSR to count how many instructions processed before

instret = 4



```
auipc a0,0x8
addi a0,a0,124 # 8100 <__sbss_end>
auipc a1,0x8
addi a1,a1,112 # 80fc <_test_start+0xfc>
li a2,0
jal ra,104 <fill_block>
```


### → RDCYCLE/RDCYCLEH

- ◆ Read CSR cycle, which is the CSR to count how many cycles processed before


31	20	19	15	14	12	11	7	6	0		
imm[11:0]		rs1		funct3		rd		opcode		Mnemonic	Description
110010000010		00000		010		rd		1110011		RDINSTRETH	rd = instret[63:32]
110000000010		00000		010		rd		1110011		RDINSTRET	rd = instret [31:0]
110010000000		00000		010		rd		1110011		RDCYCLEH	rd = cycle[63:32]
110000000000		00000		010		rd		1110011		RDCYCLE	rd = cycle[31:0]
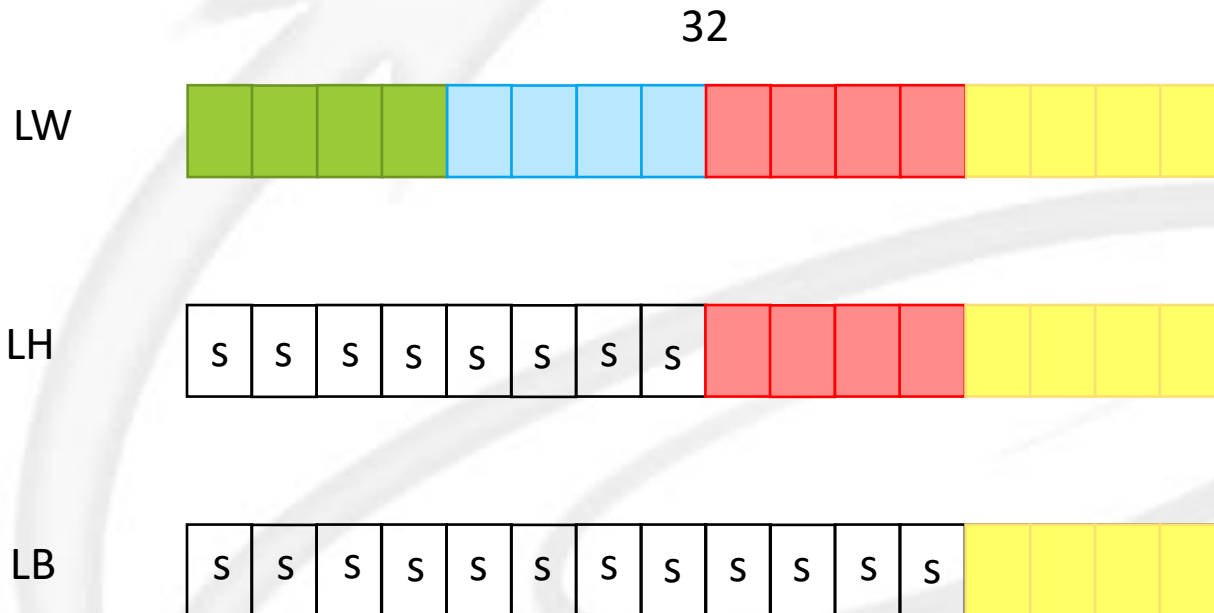
# Problem 1 – Read/Write Word/Half-word/Byte

- If the instruction is used to read half-word or bytes, all other bytes left must be filled with 0s or sign bits.



# Problem 1 – SRAM

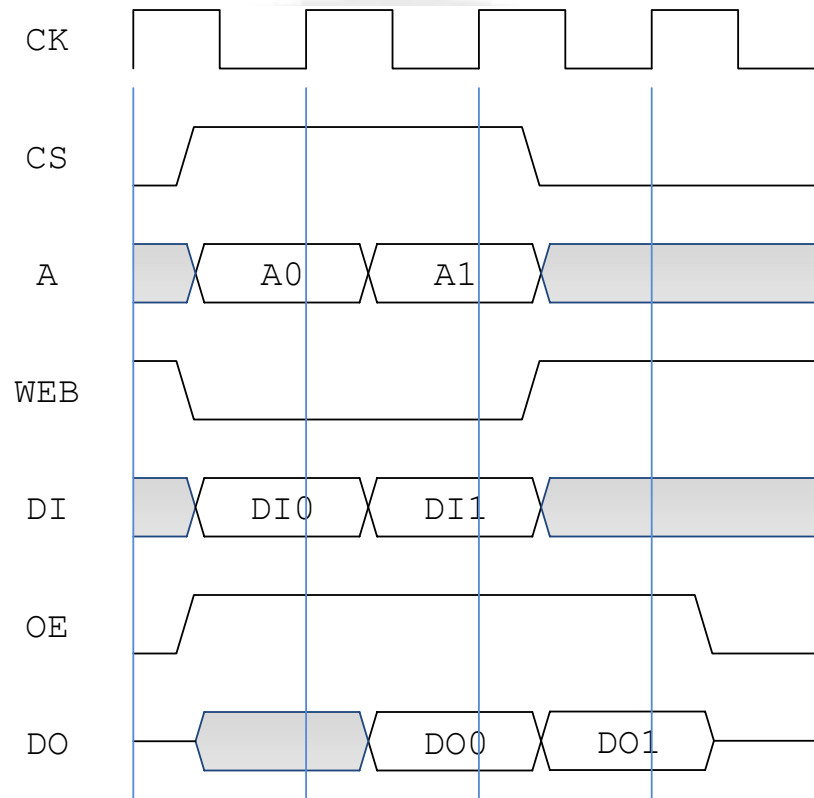

NOTE: DO delays **1 clock** after Address is imported, be aware of the pipeline registers delay



# 作業驗證說明



# Program

- prog0
  - ➔ 測試41個instruction (助教提供)
- prog1
  - ➔ Sort Algorithm
- prog2
  - ➔ Multiplication
- prog3
  - ➔ Greatest common divisor
- prog4
  - ➔ 使用階乘c code測試rdinstret, rdinstreth, rdcycle, rdcycleh(助教提供)

# Simulation

Table B-1: Simulation commands

Simulation Level	Command
Problem1	
RTL	<code>make rtl_all</code>
Post-synthesis	<code>make syn_all</code>


Table B-2: Makefile macros

Situation	Command	Example
RTL simulation for progX	<code>make rtlX</code>	<code>make rtl0</code>
Post-synthesis simulation for progX	<code>make synX</code>	<code>make syn1</code>
Dump waveform (no array)	<code>make {rtlX,synX} FSDB=1</code>	<code>make rtl2 FSDB=1</code>
Dump waveform (with array)	<code>make {rtlX,synX} FSDB=2</code>	<code>make syn3 FSDB=2</code>
Open nWave without file pollution	<code>make nWave</code>	
Open Superlint without file pollution	<code>make superlint</code>	
Open DesignVision without file pollution	<code>make dv</code>	
Synthesize your RTL code (You need write <i>synthesis.tcl</i> in <i>script</i> folder by yourself)	<code>make synthesize</code>	
Delete built files for simulation, synthesis or verification	<code>make clean</code>	
Check correctness of your file structure	<code>make check</code>	
Compress your homework to <i>tar</i> format	<code>make tar</code>	



# 作業繳交注意事項

# Testbench Structure

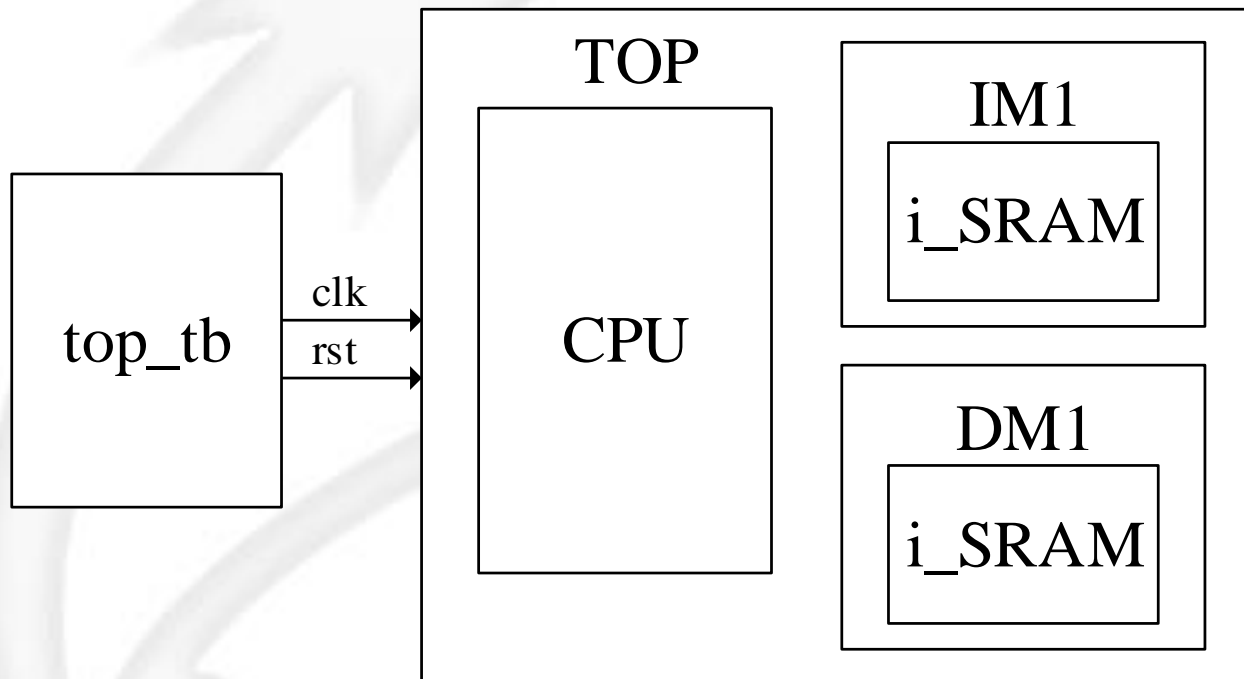



# Module (1/2)

- Module name 須符合下表要求

Category	Name			
	File	Module	Instance	SDF
RTL	top.sv	top	TOP	
RTL	SRAM_wrapper.sv	SRAM_wrapper	IM1	
RTL	SRAM_wrapper.sv	SRAM_wrapper	DM1	
RTL	SRAM_rtl.sv	SRAM	i_SRAM	

- 紫色部分為助教已提供或已定義好，請勿任意更改
- 其餘部分需按照要求命名，以免testbench抓不到正確的名稱

## Module (2/2)


Module port 須符合下表要求

Module	Specifications			
	Name	Signal	Bits	Function explanation
top	clk	input	1	System clock
	rst	input	1	System reset (active high)
SRAM_wrapper	CK	input	1	System clock
	CS	input	1	Chip select (active high)
	OE	input	1	Output enable (active high)
	WEB	input	4	Write enable (active low)
	A	input	14	Address
	DI	input	32	Data input
	DO	output	32	Data output
SRAM	Memory Space			
	Memory_byte0	logic	8	Size: [16384]
	Memory_byte1	logic	8	Size: [16384]
	Memory_byte2	logic	8	Size: [16384]
	Memory_byte3	logic	8	Size: [16384]

- 紫色部分為助教已提供或已定義好，請勿任意更改
- 其餘部分需按照要求命名，以免testbench抓不到正確的名稱
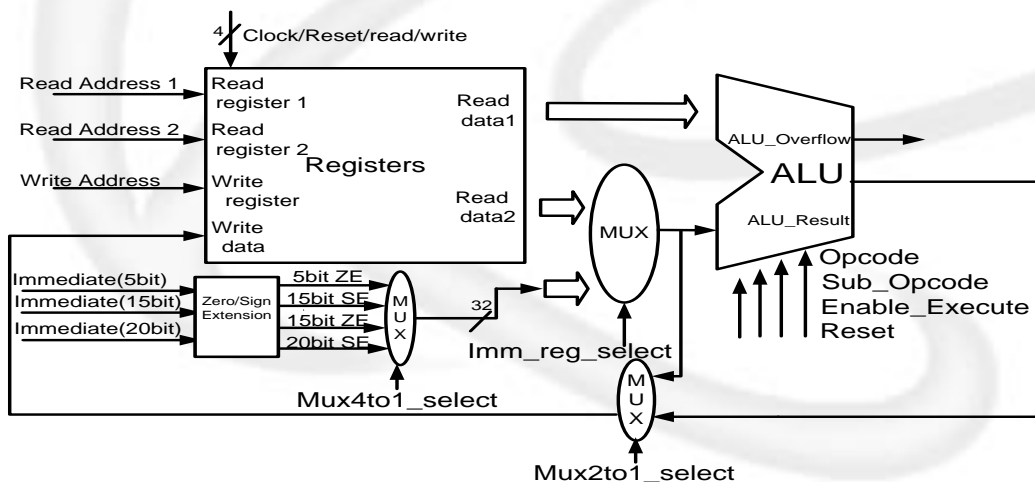
# Report (1/2)

- ❑ 請勿將code貼在.docx內
  - ➔ 請將.sv包在壓縮檔內，不可截圖於.docx中
- ❑ 需要Summary及Lessons learned
- ❑ Block diagram
  - ➔ 不必畫到gate level，除非該處的邏輯對於設計上有重要意義
  - ➔ 可用一個矩形標上名稱以及I/O代表一個 functional block
  - ➔ 呈現要點在於讓人較容易理解你的設計的架構
  - ➔ 可以使用Visio、Open Office Draw，或其他繪圖軟體



## Report (2/2)

### □ 驗證波形圖


- 保留完整訊號名稱以及訊號值
- 輔以文字解釋該波形圖的操作
- 可在波形圖加上標示輔助了解
- 截圖裁減至合適大小

v. 測試AND的功能。當enable\_execute為1時，表示alu開始做運算，opcode為100000，sub\_opcode為00010，動作為AND。

scr1=32' b1100\_0101\_1010\_1111\_1000\_0101\_1010\_1001，

scr2=32' b1111\_1010\_0101\_0000\_1110\_0101\_1010\_1111，

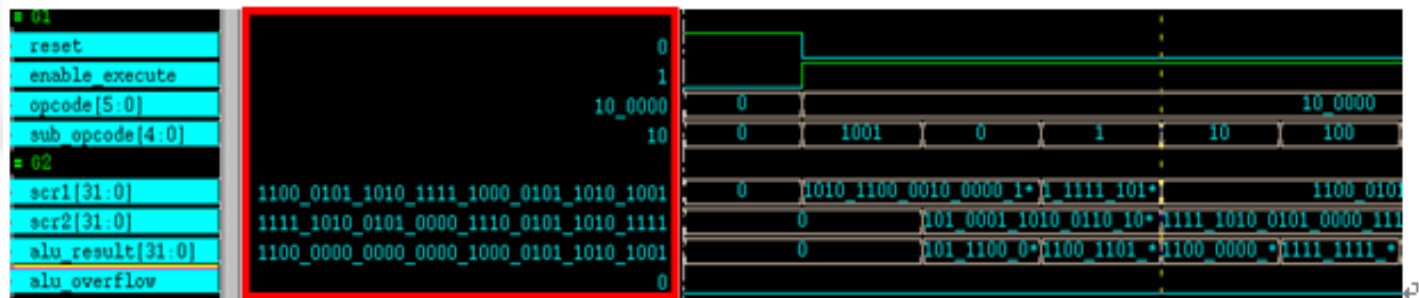結果為=32' b1100\_0000\_0000\_0000\_1000\_0101\_1010\_1001。





# 繳交檔案

- 依照檔案結構壓縮成 “.tar” 格式
  - ➔ 在Homework主資料夾(N260XXXXX)使用make tar產生的tar檔即可符合要求
- 檔案結構請依照作業說明
- 請勿附上檔案結構內未要求繳交的檔案
  - ➔ 在Homework主資料夾(N260XXXXX)使用make clean即可刪除不必要的檔案
- 請務必確認繳交檔案可以在SoC實驗室的工作站下compile，且功能正常
- 無法compile將直接以0分計算
- 請勿使用generator產生code再修改
- 禁止抄襲

# 檔案結構 (1/2)

- N260XXXXX.docx  
→ Your report file
- src  
→ Your source code (\*.sv)
- include  
→ Your definition code (\*.svh)
- StudentID  
→ Specify your Student ID number
- sim/CYCLE  
→ Specify your clock cycle time
- sim/MAX  
→ Specify max clock cycle number

- *N260XXXXX.tar* (Don't add version text in filename, e.g. *N260XXXXX\_v1.tar*)
  - *N260XXXXX* (Main folder of this homework)
    - *N260XXXXX.docx* (Your homework report)
    - *StudentID* (Specify your student ID number in this file)
    - *Makefile* (You shouldn't modify it)
    - *src* (Your RTL code with sv format)
      - *top.sv*
      - *SRAM\_wrapper.sv*
      - Other submodules (\*.sv)
    - *include* (Your RTL definition withsvh format, optional)
      - Definition files (\*.svh)
    - *syn* (Your synthesized code and timing file, optional)
      - *top\_syn.v*
      - *top\_syn.sdf*
    - *script* (Any scripts of verification, synthesis or place and route)
      - Script files (\*.sdc, \*.tcl or \*.setup)
    - *sim* (Testbenches and memory libraries)
      - *top\_tb.sv* (Main testbench. You shouldn't modify it)
      - *CYCLE* (Specify your clock cycle time in this file)
      - *MAX* (Specify max clock cycle number in this file)
      - *SRAM* (SRAM libraries and behavior models)
        - Library files (\*.lib, \*.db, \*.lef or \*.gds)
        - *SRAM.ds* (SRAM datasheet)
        - *SRAM\_rtl.sv* (SRAM RTL model)
        - *SRAM.v* (SRAM behavior model)

# 檔案結構 (2/2)

## □ sim/prog0 、 sim/prog4

→ Don't modify contents

## □ sim/progX (X ≠ 0,4)

→ main.S

→ main.c

◆ Submit one of these

- ✚ *prog4* (Subfolder for Program 4)
  - *Makefile* (Compile and generate memory content)
  - *main.c* (C code for verification)
  - *data.S* (Assembly code for testing data)
  - *setup.S* (Assembly code for testing environment setup)
  - *link.ld* (Linker script for testing environment)
  - *golden.dat* (Golden hexadecimal data)

- ✚ *SRAM* (SRAM libraries and behavior models)
  - Library files (\*.lib, \*.db, \*.lef or \*.gds)
  - *SRAM.ds* (SRAM datasheet)
  - *SRAM\_rtl.sv* (SRAM RTL model)
  - *SRAM.v* (SRAM behavior model)
- ✚ *prog0* (Subfolder for Program 0)
  - *Makefile* (Compile and generate memory content)
  - *main.S* (Assembly code for verification)
  - *setup.S* (Assembly code for testing environment setup)
  - *link.ld* (Linker script for testing environment)
  - *golden.hex* (Golden hexadecimal data)
- ✚ *prog1* (Subfolder for Program 1)
  - *Makefile* (Compile and generate memory content)
  - *main.S* \* (Assembly code for verification)
  - *main.c* \* (C code for verification)
  - *data.S* (Assembly code for testing data)
  - *setup.S* (Assembly code for testing environment setup)
  - *link.ld* (Linker script for testing environment)
  - *golden.hex* (Golden hexadecimal data)
- ✚ *prog2* (Subfolder for Program 2)
  - *Makefile* (Compile and generate memory content)
  - *main.S* \* (Assembly code for verification)
  - *main.c* \* (C code for verification)
  - *data.S* (Assembly code for testing data)
  - *setup.S* (Assembly code for testing environment setup)
  - *link.ld* (Linker script for testing environment)
  - *golden.hex* (Golden hexadecimal data)
- ✚ *prog3* (Subfolder for Program 3)
  - *Makefile* (Compile and generate memory content)
  - *main.S* \* (Assembly code for verification)
  - *main.c* \* (C code for verification)
  - *data.S* (Assembly code for testing data)
  - *setup.S* (Assembly code for testing environment setup)
  - *link.ld* (Linker script for testing environment)
  - *golden.hex* (Golden hexadecimal data)

# 繳交期限

- 2022/10/05 (三) 14:00前上傳
  - ➔ 不接受遲交，請務必注意時間
  - ➔ Moodle只會留存你最後一次上傳的檔案，檔名只要是「**N260XXXXX.tar**」即可，不需要加上版本號
- 作業二預計在2022/10/05 (三)會上傳，請務必加快作業一的設計時間，以免壓縮到作業二的時間



# 注意事項

- 本次作業**合成**的部分有計入PA(Performance & Area)，表現較為優異者將有較高的評分(30%)
- 作業部分有任何問題請在**moodle上的作業討論區**發問並可參考其他人是否有類似的問題，助教信箱恕不回覆。
- 在Script/DC.sdc中，可以更改clk period範圍，請注意最大的接受值為**20.0**，超過此範圍者恕不納入計分。此外，若有更改預設clock period者，請務必更改set\_input\_delay -max至1/2 clk period，以利後續作業的合成及模擬。
- 本次作業需在SoC環境下模擬，請同學務必在SoC教室執行模擬，若是助教在評分作業時於SoC無法成功模擬則以0分計算。

**Thanks for your participation and  
attendance !!**